

## Quiz 2

① Draw the truth table for the boolean function representing the following algebraic expressions.

- a)  $1 - xy$
- b)  $x^2 + y$

[2+2]

② Consider the following ckt:

- a) What is the size?
- b) What is the min. no. of bits reqd. to represent a gate in the ckt (including leaves)?
- c) Redraw the ckt and assign names to the non-haf gates.  
What have you named the root?
- d) Assign strings (of length calculated in (b)) to represent the gates (including leaves).
- e) Let us represent  $\neg \equiv 00$ ,  $\wedge \equiv 01$ ,  $\vee \equiv 10$ .  
Use this and (d) to give a string representation of the ckt.

[1+1+3+3+8]

